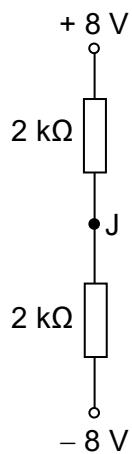
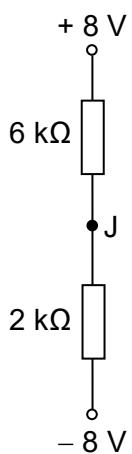
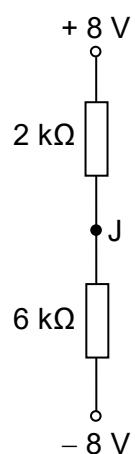


In which arrangement is the potential at J equal to -4 V ?

A**B****C****D**