

- 3 A battery is connected with resistors R , X and Y , as shown in Fig. 3.1.

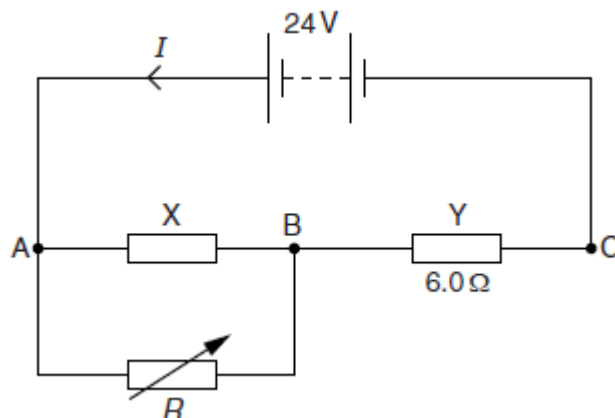


Fig. 3.1

The resistance of X is constant. The resistance of Y is $6.0\ \Omega$. The battery has electromotive force (e.m.f.) 24 V and zero internal resistance. A variable resistor of resistance R is connected in parallel with X .

The current I from the battery is changed by varying R from $5.0\ \Omega$ to $20\ \Omega$. The variation with R of I is shown in Fig. 3.2.

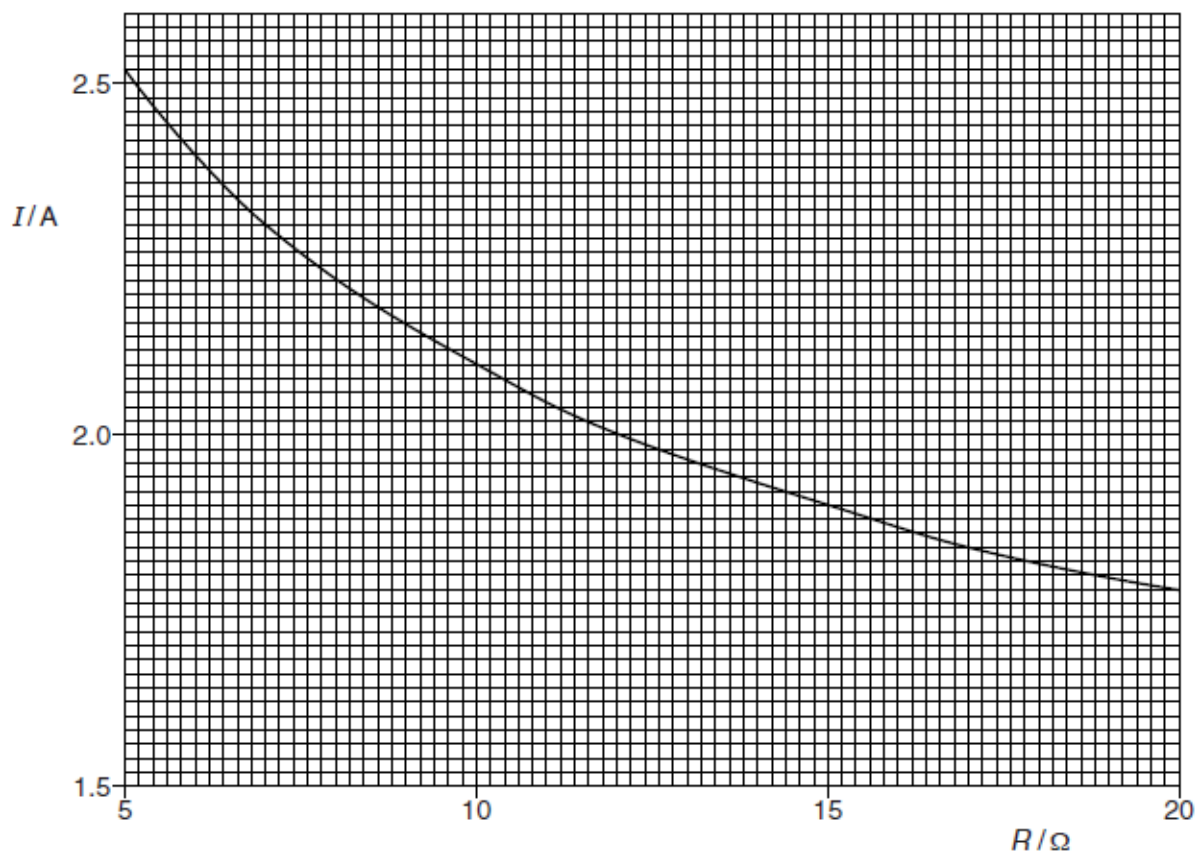


Fig. 3.2

- (a) Explain why the potential difference (p.d.) between points A and C is 24 V for all values of R .

.....
 [1]

- (b) Use Fig. 3.2 to state and explain the variation of p.d. across resistor Y as R is increased. Numerical values are not required.

.....

 [2]

- (c) For $R = 6.0 \, \Omega$,

- (i) show that the p.d. between A and B is 9.6 V,

[2]

- (ii) calculate the resistance of X,

resistance = Ω [3]

- (iii) calculate the power provided by the battery.

power = W [1]

- (d) State and explain qualitatively how the power provided by the battery changes as the resistance R is increased.

.....
 [1]

[Total: 10]