

- 20** A metal cube has a resistance of $4.0\ \Omega$ between opposite faces. Ten of these cubes are put together to make a cuboid as shown.



There is no extra resistance where the faces of the cubes touch each other.

What is the resistance of the cuboid when connected between faces X and Y?

- A** $1.6\ \Omega$
- B** $2.0\ \Omega$
- C** $10\ \Omega$
- D** $40\ \Omega$