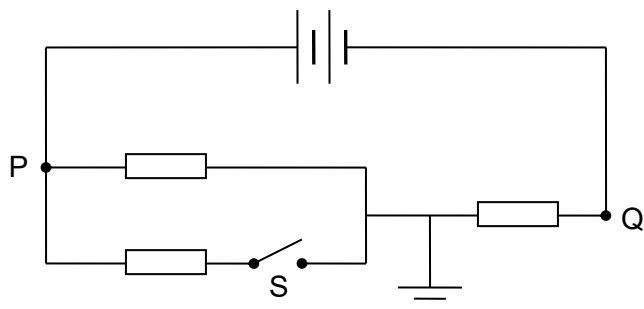


- 21 A group of resistors are connected as shown to a battery of constant e.m.f. with negligible internal resistance. All resistors have the same resistances.



What will happen to the potentials at P and at Q when the switch S is closed?

	potential at P	potential at Q
A	unchanged	unchanged
B	increased	increased
C	decreased	increased
D	decreased	decreased