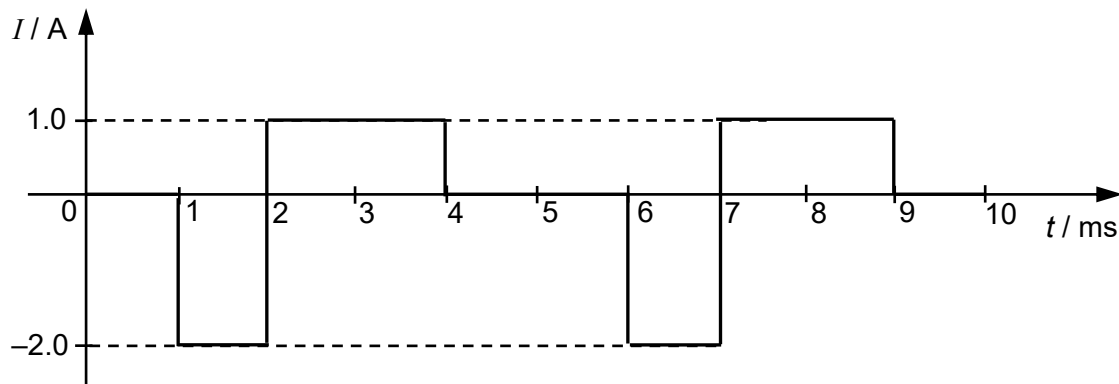


- 26** An alternating current with a rectangular waveform as shown in the diagram below flows through a $10\ \Omega$ resistor.



What is the average power dissipated by the resistor?

- A** $0\ \text{W}$ **B** $8\ \text{W}$ **C** $12\ \text{W}$ **D** $28\ \text{W}$

[Turn over