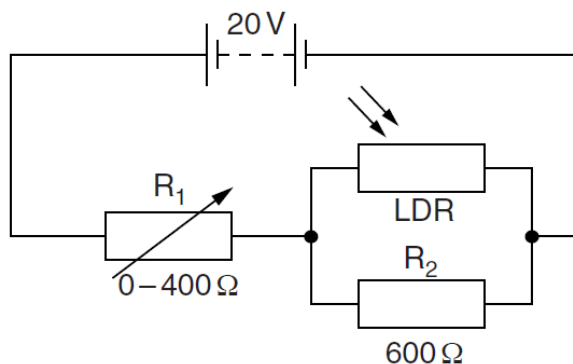


6

(a)

A light-dependent resistor (LDR) is connected to a variable resistor  $R_1$  and a fixed resistor  $R_2$ , as shown in Fig. 6.1.



**Fig. 6.1**

When the light intensity is varied, the resistance of the LDR changes from  $5.0 \text{ k}\Omega$  to  $1.2 \text{ k}\Omega$ .


(i)

For the maximum light intensity, calculate the total resistance of  $R_2$  and the LDR.

total resistance = .....  $\Omega$  [2]

(ii)


Fig 6.2 shows the circuit when the LDR is removed.

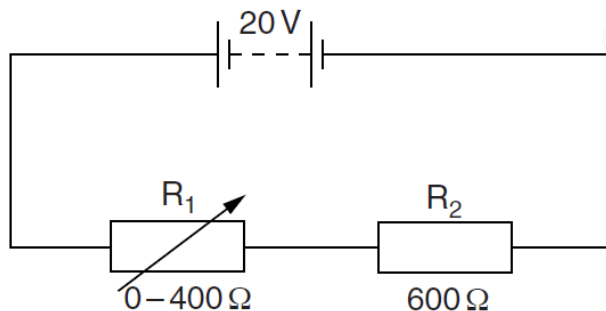

**Fig. 6.2**


The resistance of  $R_1$  is varied from 0 to  $400\ \Omega$  in the circuits of Fig. 6.1 and Fig. 6.2. State and explain the difference, if any, between the minimum potential difference across  $R_2$  in each circuit. Numerical values are not required.

 .....  
 .....  
 .....  
 .....  
 ..... [3]



**(b)**

In Fig. 6.3, XZ is a uniform metre wire and has a resistance of  $10.0\ \Omega$ . E is a power supply of electromotive force (e.m.f.)  $2.0\ \text{V}$  with negligible internal resistance. The resistor  $R_1$  has a resistance of  $15.0\ \Omega$  and the resistor  $R_2$  has a resistance of  $5.0\ \Omega$ .

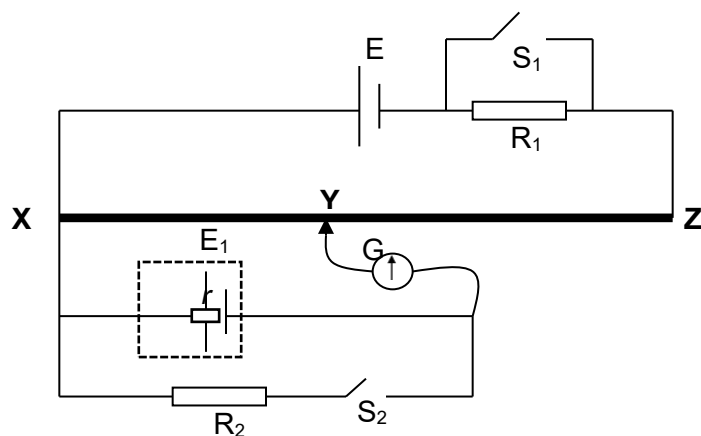

**Fig. 6.3**

With both switches  $S_1$  and  $S_2$  open, length YZ is 37.5 cm when galvanometer G registers null deflection.

When  $S_1$  and  $S_2$  are closed, length YZ is 90.0 cm when galvanometer G registers null deflection.



**(i)**

Show that the e.m.f. of cell  $E_1$  is 0.50 V.

[3]



**(ii)**

Determine the internal resistance  $r$  of cell  $E_1$ .

$r = \dots\dots\dots\Omega$  [3]

[Total: 11]