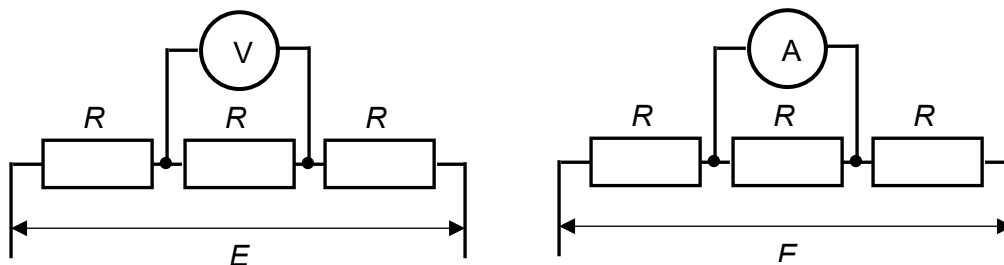


- 23** Three identical resistors of resistance $10\ \Omega$ are connected in series with a constant voltage supply E . The reading on an ideal voltmeter connected across R_2 is $5.0\ \text{V}$.



What will be the reading on an ideal ammeter if it is connected across R_2 ?

- A** $0.25\ \text{A}$ **B** $0.50\ \text{A}$ **C** $0.75\ \text{A}$ **D** $1.5\ \text{A}$