

- 4 A thermistor is connected in series with a fixed resistor of  $1.20\text{ k}\Omega$  and a battery, as shown in Fig 4.1. The e.m.f.  $E$  of the battery is unknown and its internal resistance is negligible.

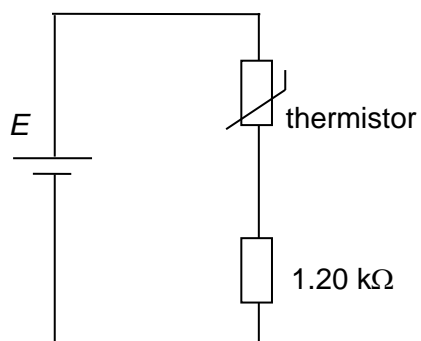


Fig. 4.1

The variation with temperature  $\theta$  of the resistance  $R$  of the thermistor is shown in Fig. 4.2.

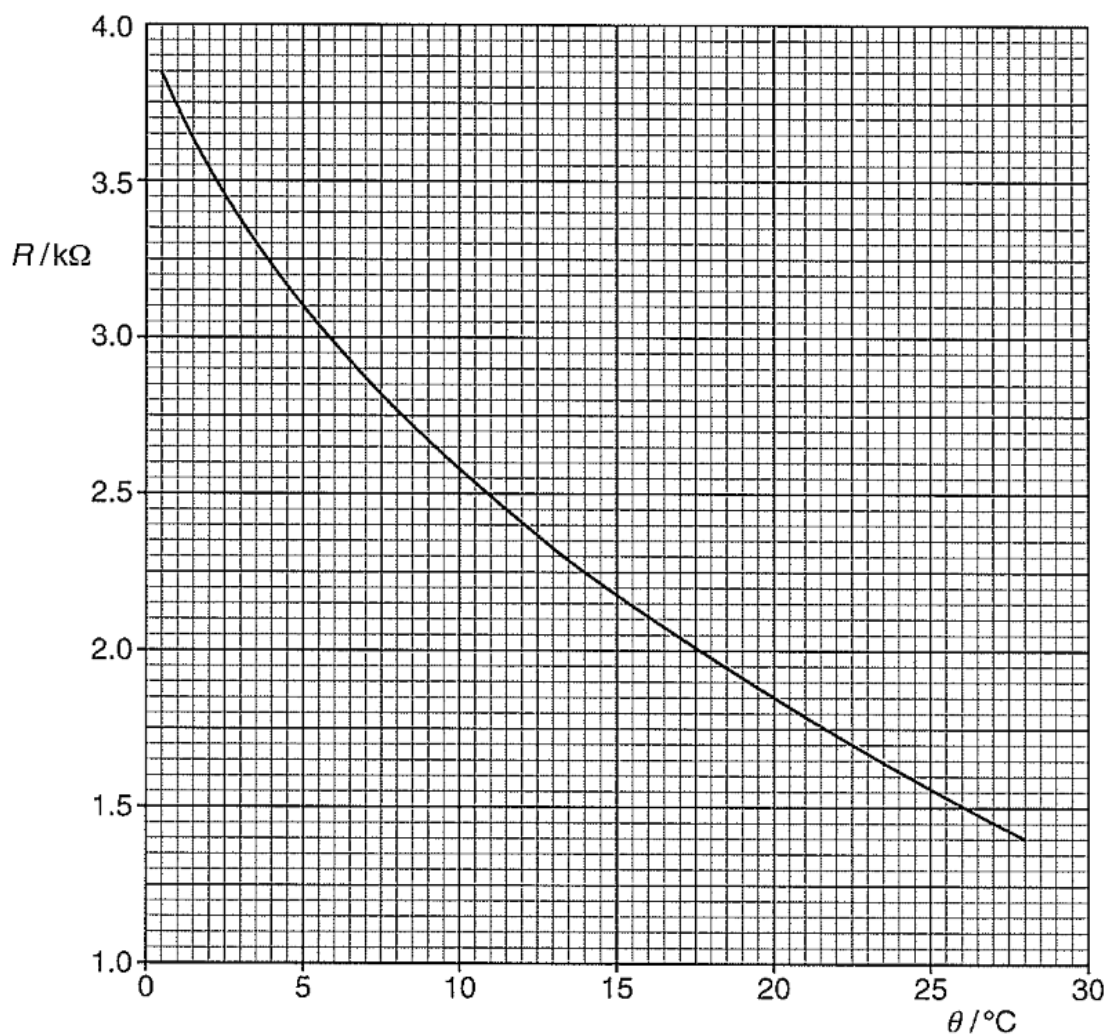


Fig. 4.2

The thermistor is immersed in a liquid maintained at a constant temperature of  $5.0\text{ }^{\circ}\text{C}$ . The energy delivered by the battery is  $11.3\text{ J}$  for a duration of  $10.0\text{ min}$ .

- (a) (i) Determine the power delivered by the battery.

power = ..... W [2]

- (ii) Hence, determine the e.m.f.  $E$  of the battery.

$E = \dots\dots\dots\text{ V}$  [3]

- (b) The thermistor is removed and immersed in another liquid maintained at a constant temperature of  $17.5\text{ }^{\circ}\text{C}$ . The fixed resistor is replaced with another fixed resistor with a different resistance.

If the battery delivers the same power as before, determine the resistance of the fixed resistor.

resistance = .....  $\Omega$  [3]

[Total: 8]