
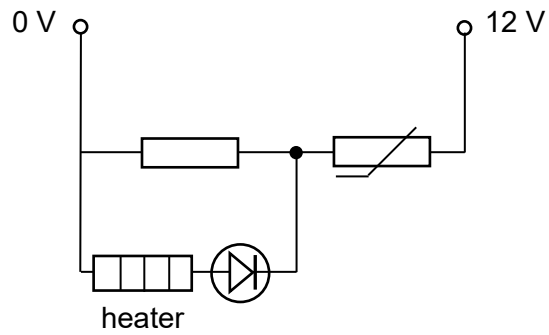


- 23** A circuit is needed to turn on a heater when the temperature of a thermistor is too low. Which of the following circuits is suitable?


A

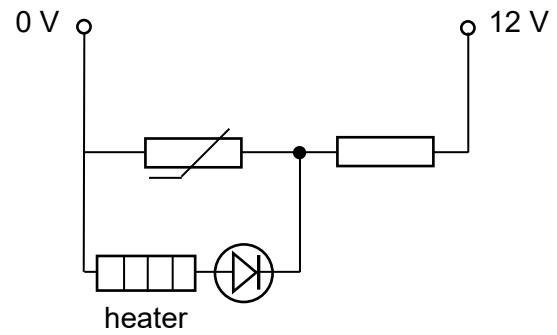

B



C

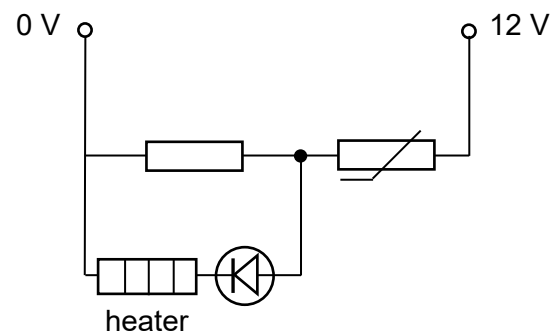

D

