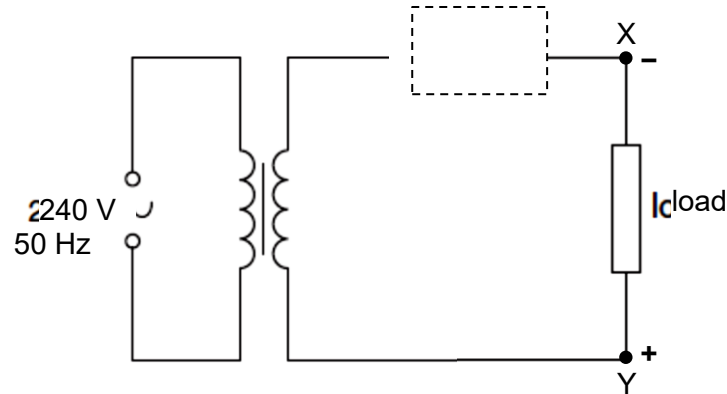


- 6 A student uses a 240 V, 50 Hz sinusoidal alternating supply, a transformer and a diode to design a circuit. The circuit produces a direct voltage of peak value 6.0 V across a load of resistance  $4.0\ \Omega$ . Both the transformer and diode can be assumed to be ideal.

The partially completed circuit diagram is shown in Fig. 6.1.



**Fig. 6.1**

- (a) In the dotted box of Fig. 6.1, draw the symbol representing the diode that needs to be connected such that Y has a higher potential than X across the load.

[1]

- (b) The root-mean-square (r.m.s.) voltage of the alternating supply is 240 V.

Explain what is meant by root-mean-square voltage.


.....  
 .....  
 ..... [1]

- (c) Calculate the ratio

$$\frac{\text{number of turns on the secondary coil}}{\text{number of turns on the primary coil}}.$$

ratio = ..... [2]

- (d) On Fig. 6.2, sketch a graph to show for the load, the variation with time  $t$  of the potential of X with respect to Y ( $V_{XY}$ ) for up to  $t = 0.060$  s.

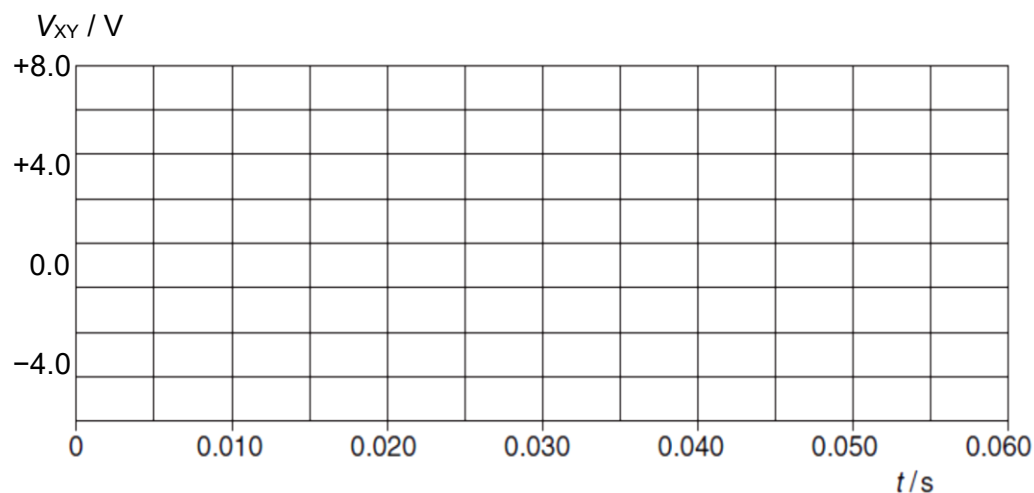

**Fig. 6.2**

[2]

- (e) Calculate, for the load,

- (i) the r.m.s. voltage,

r.m.s. voltage = ..... V [1]

- (ii) the mean power dissipated.

mean power = ..... W [1]

