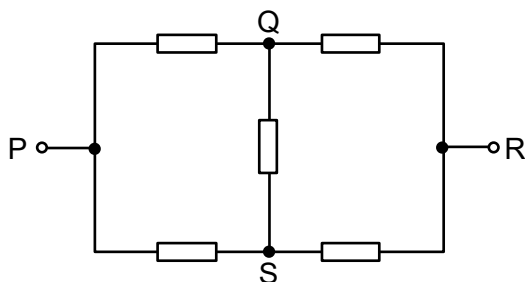


- 24** A current flows from P to R through a network of resistors such that the potential differences (p.d.) across PQ, QR and PS are 3 V, 5 V and 6 V respectively.



Which row is correct?

	p.d. across SR	p.d. across QS
<b>A</b>	2 V	3 V
<b>B</b>	3 V	2 V
<b>C</b>	8 V	3 V
<b>D</b>	10 V	2 V