

- 5 (a) Define *resistance* of a circuit component.

.....

..... [1]

- (b) Fig. 5.1 shows a potential divider circuit consisting of two resistors of resistances A and B .

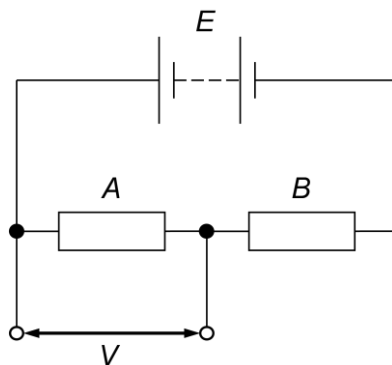


Fig. 5.1

The battery has an e.m.f. E and negligible internal resistance.

By considering the current in circuit, show that the potential difference V across the resistor of resistance A is given by the expression

$$V = \frac{A}{A+B} E$$

[1]

[Turn over

- (c) The resistances A and B are $1500\ \Omega$ and $4000\ \Omega$ respectively. A voltmeter is connected in parallel with the $1500\ \Omega$ resistor and a thermistor is connected in parallel with the $4000\ \Omega$ resistor, as shown in Fig. 5.2.

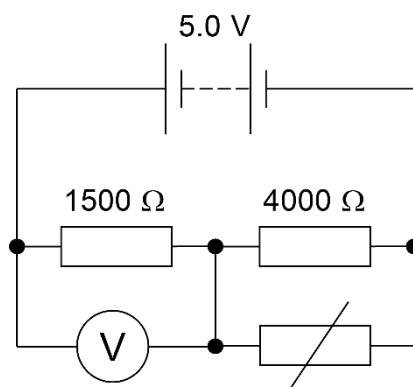


Fig. 5.2

The battery has an e.m.f. of 5.0 V and the voltmeter is ideal.

- (i) State and explain the change in the reading of the voltmeter as the temperature of the thermistor is raised.

.....

 [3]

- (ii) The resistance of the thermistor at $20\ ^\circ\text{C}$ is $2700\ \Omega$.

Calculate the reading on the voltmeter when the temperature of the thermistor is $20\ ^\circ\text{C}$.

voltmeter reading = V [3]

- (iii) For the same change in temperature, state and explain how the change in the voltmeter reading will be different if the battery has significant internal resistance.

.....

.....

.....

..... [2]