

- 27** An alternating current I (in amperes) varies with time t (in seconds) according to the equation
$$I = 5 \sin(100\pi t).$$

What is the mean power developed by the current in a resistive load of $10 \, \Omega$?

- A** 125 W **B** 160 W **C** 250 W **D** 500 W