

- 27 Which of the following graphs best represents the variation with time  $t$  of the current  $I$  through the  $200\ \Omega$  resistor in the circuit below?



