

- 7 (a) Fig. 7.1 shows the variation with potential difference V of the current I for a filament lamp X rated at 6.0 V and 1.5 W.

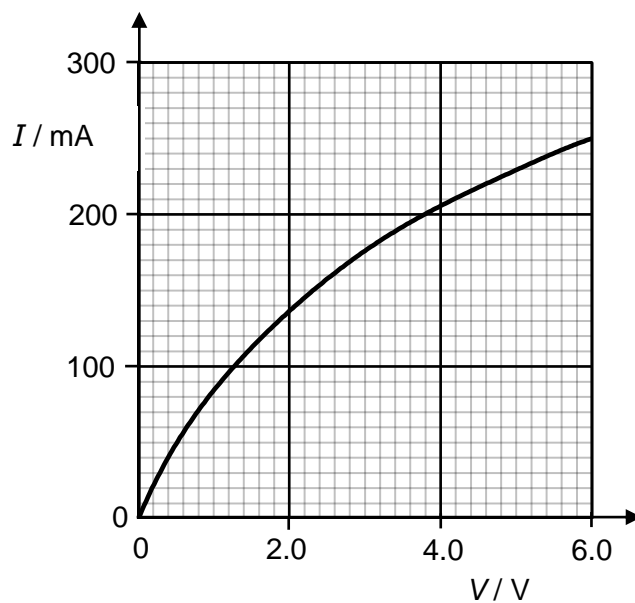


Fig. 7.1

- (i) Calculate the resistance of the filament lamp at 6.0 V.

resistance = Ω [2]

- (ii) Explain how Fig. 7.1 shows that the resistance of the filament lamp increases as the potential difference across the filament lamp increases.

.....
..... [1]

- (iii) The filament lamp X is connected in series with a battery B and a variable resistor R, and, in parallel with a voltmeter, as shown in Fig. 7.2.

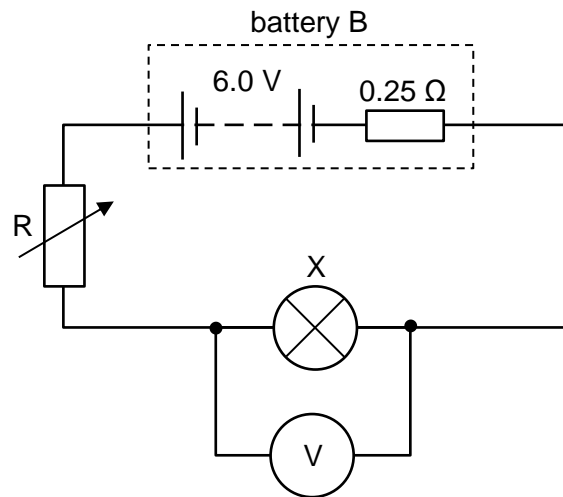


Fig. 7.2

Battery B has electromotive force 6.0 V and internal resistance 0.25 Ω.

The resistance of R is adjusted such that the voltmeter reads 5.0 V.

Calculate the terminal potential difference (p.d.) across B. Show your working.

terminal p.d. across B = V [3]

- (b) Fig. 7.3(a) and Fig. 7.3(b) show two circuits which can be used to act as a dimmer switch for a lamp.

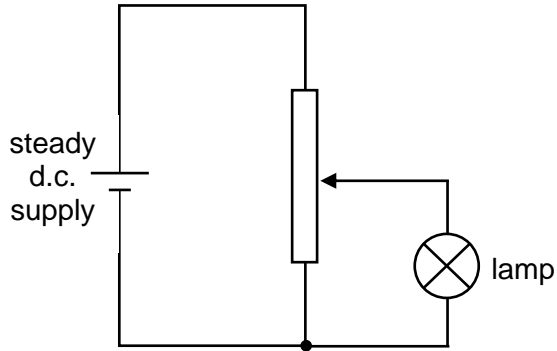


Fig. 7.3(a)

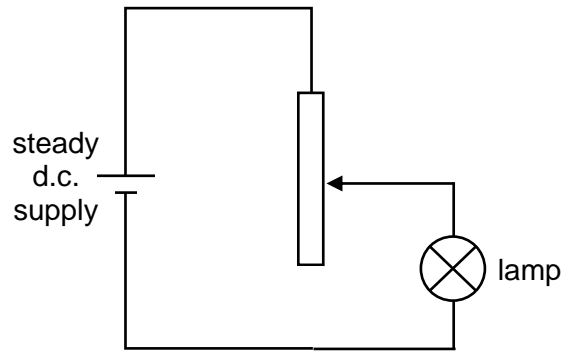


Fig. 7.3(b)

State and explain one advantage the circuit in Fig. 7.3(a) has over the circuit in Fig. 7.3(b) in varying the brightness of the lamp.

.....

.....

..... [2]