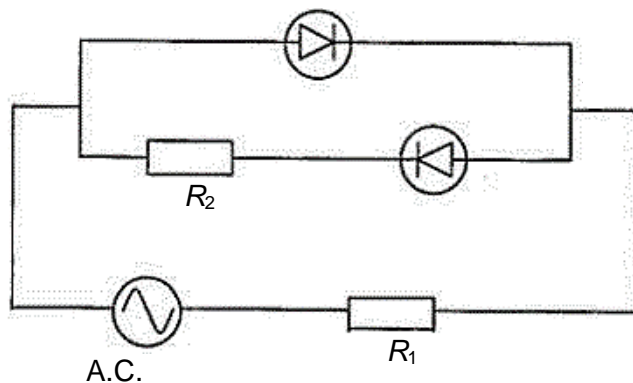


- 25 A circuit consists of an a.c. supply, two diodes, and two resistors with resistance R_1 and R_2 respectively.



Which of the following graphs represents the variation of current I with time t through R_1 of the circuit?

