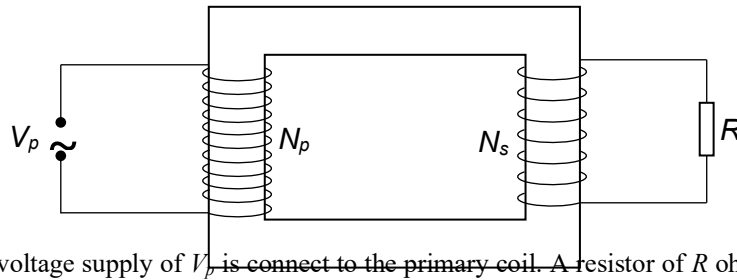


- 25 The figure below shows an ideal transformer with  $N_p$  turns in its primary coil and  $N_s$  turns in its secondary coil.



An alternating voltage supply of  $V_p$  is connect to the primary coil. A resistor of  $R$  ohms is connected to the secondary coil.

Which expression gives the power in the primary coil?

- A  $\frac{N_p^2 V_p}{N_s^2 R}$       B  $\frac{N_s V_p^2}{N_p R}$       C  $\frac{N_s^2 V_p^2}{N_p^2 R}$       D  $\frac{N_s^2 V_p}{N_p^2 R}$