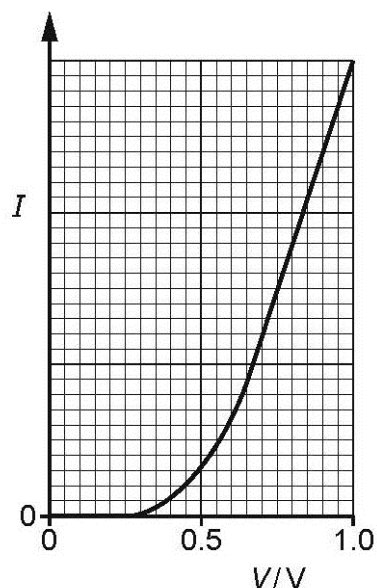


- 6 (a) The variation with potential difference  $V$  of the current  $I$  in a semiconductor diode  
) is shown in Fig. 6.1.



**Fig. 6.1**

Use Fig. 6.1 to describe qualitatively,


- (i) the resistance of the diode in the range  $V = 0$  to  $V = 0.25$  V.

..... [1]  
..... ]

- (ii) the variation, if any, in the resistance of the diode as  $V$  changes from  $V = 0.75$  V to  $V = 1.0$  V.

..... [1]  
..... ]

- (b) A battery of electromotive force (e.m.f.) 9.0 V and negligible internal resistance is  
) connected to a uniform resistance wire XY, a galvanometer, a light-dependent resistor (LDR) and a fixed resistor of  $1200\ \Omega$ , as shown in Fig. 6.2.

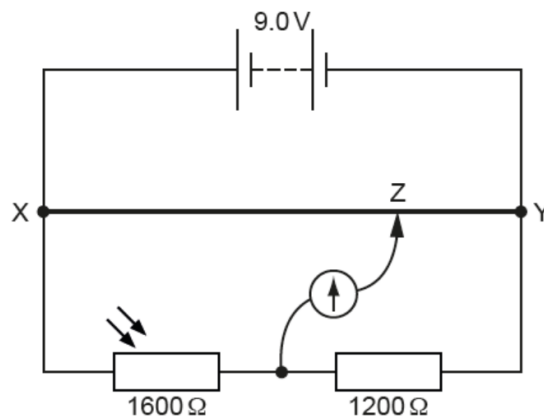

**Fig. 6.2**

The length of the wire XY is 1.2 m. The movable connection Z is positioned on the wire XY so that the galvanometer gives a zero reading.

- (i) Calculate the length XZ along the resistance wire when the LDR has a resistance of  $1600\ \Omega$ .

length XZ = ..... m [2  
]

- (ii) The intensity of the light illuminating the LDR is now increased.

State and explain whether there is a decrease, increase or no change to:

1. the length XZ so that the galvanometer reads zero.

.....  
.....

.....  
.....

..... [2  
..... ]

.....  
.....

2. the total power supplied by the battery.

.....  
.....

.....  
.....

..... [2  
..... ]

.....  
.....

[Total: 8]

