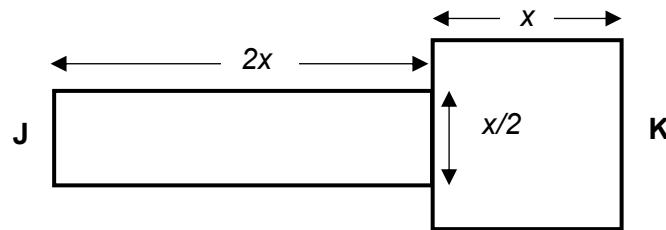


- 21 A thin rectangular sheet of metal of uniform thickness and of length $2x$ and width $\frac{x}{2}$ is connected to another square sheet of the same metal of the same thickness, which has a resistance of 8.0Ω measured between opposite edges.



What is the resistance between edges **J** and **K**?

- A 6.4Ω B 16Ω C 32Ω D 40Ω