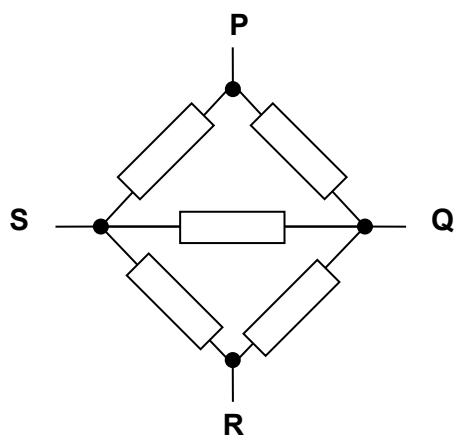


- 23** Five resistors of equal resistance are connected as shown.



Which two points would give the maximum resistance?

- |          |    |          |    |
|----------|----|----------|----|
| <b>A</b> | PQ | <b>B</b> | PR |
| <b>C</b> | PS | <b>D</b> | QS |