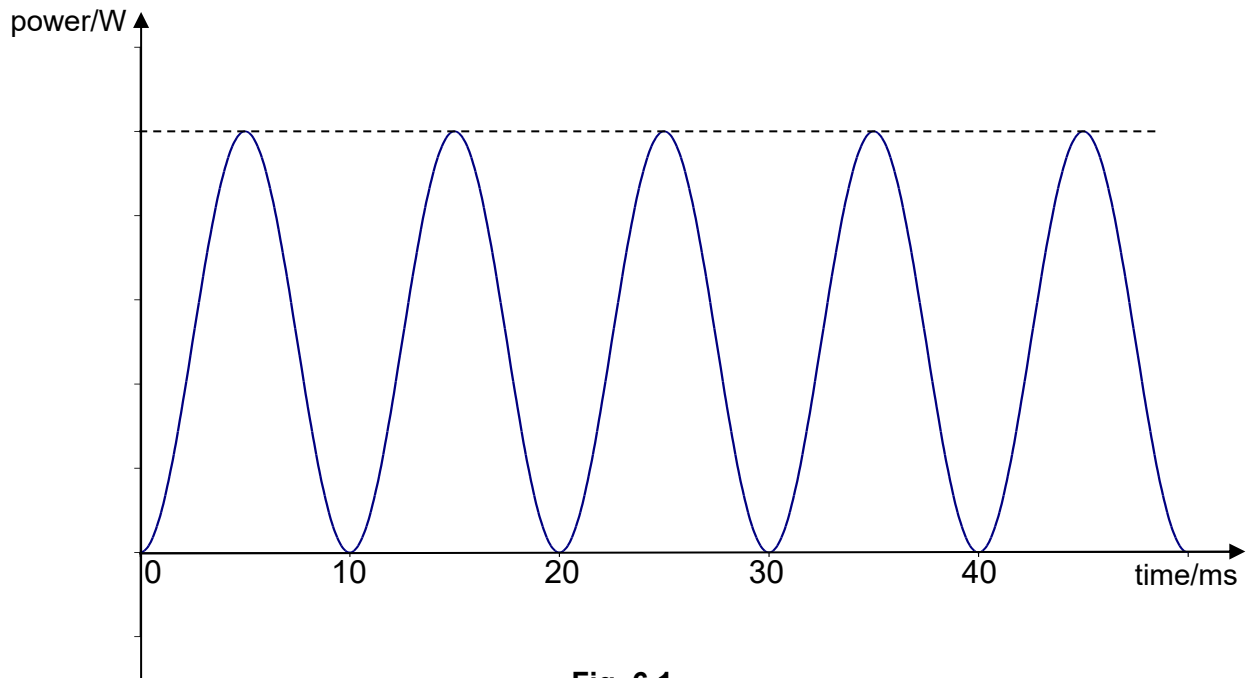


- 6 A transformer has a turns ratio of $N_p/N_s = 1/20$ and the sinusoidal input signal voltage has a value of 9.0 V r.m.s. The mean power input to the transformer is 30 W. A graph of the power input is shown in Fig. 6.1.



The output of the transformer is connected across a resistor R.

(a) For the transformer, assumed to be ideal, calculate

(i) the r.m.s. value of the output voltage,

r.m.s. output voltage =V [1]

(ii) the r.m.s. value of the input current,

r.m.s. input current =A [1]

- (iii) State the equation of the variation with time t of the output voltage V .

[2]

- (b) A diode is inserted in series with the resistor R .

State

- (i) the peak power dissipated in R ,

peak power =W [1]

- (ii) the mean power dissipated in R .

mean power =W [1]

- (c) (i) Explain why thermal energy is generated in the core when the transformer is in use.

.....

 [2]

- (ii) State a typical feature in the design of the iron core to reduce power loss.

..... [1]