

- 21** A fixed resistor and a diode are combined by connecting them in series. The total potential difference  $V$  across the combination is varied and the corresponding current  $I$  is measured.

Which graph could represent the variation of  $I$  with  $V$ ?

