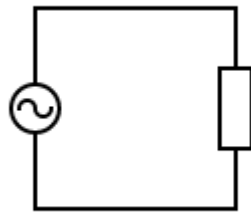
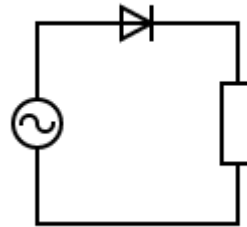


- 27 A circuit with a sinusoidal alternating power supply is rectified with a diode as shown.



before rectification



after rectification

The mean power of the circuit before rectification is P .

What is the peak and mean power of the circuit after rectification?

| | peak power | mean power |
|----------|------------|------------|
| A | $0.5P$ | $0.5P$ |
| B | P | $0.5P$ |
| C | $2P$ | $0.5P$ |
| D | $2P$ | P |