

- 2 (a)** A piece of resistance wire PQ of length 120 cm and diameter 1.1 mm has resistivity $1.1 \times 10^{-6} \Omega \text{ m}$.

(i) Show that the resistance of the wire PQ is 1.4Ω . [1]

- (ii)** Wire PQ is now connected to a circuit as shown in Fig. 2.1 below. A voltmeter is connected to point X and Y, where X is the mid-point between PQ.

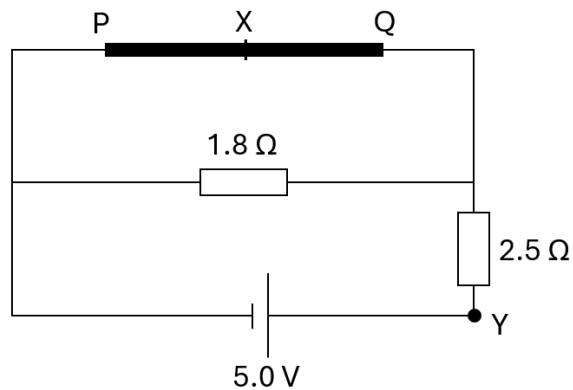


Fig. 2.1

Determine the reading on the voltmeter.

voltmeter reading = V [3]

- (b) Two long straight parallel wires A and B carrying currents I_A and I_B respectively are positioned 5.0 cm apart as shown in Fig. 2.2. Currents I_A and I_B are directed along the same direction.

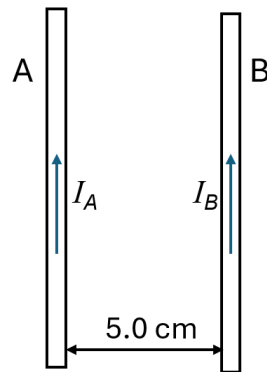


Fig. 2.2

- (i) Explain why the two wires are attracted to one another.

.....

 [2]

- (ii) The currents are now replaced with alternating currents.

I_A is represented by the equation:

$$I_A = -3.0 \cos(200\pi t)$$

I_B is represented by the graph shown in Fig. 2.3.

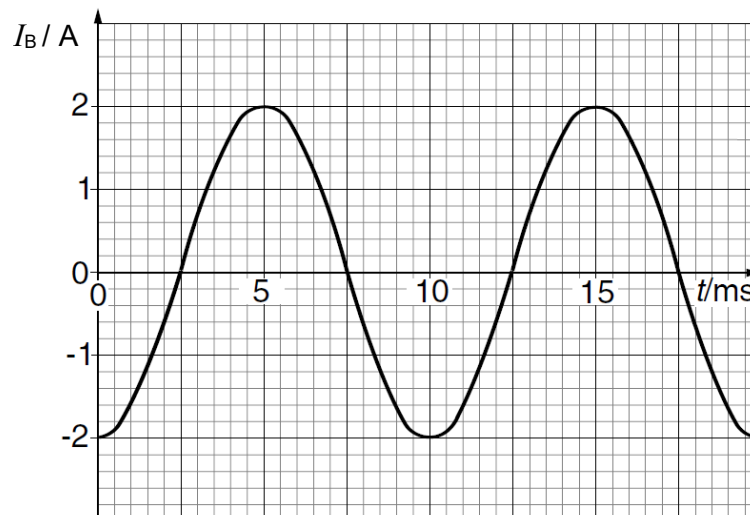


Fig. 2.3

1. Determine the instantaneous force per unit length acting on wire A when $t = 6.5$ ms.

force per unit length = N m^{-1} [3]

2. A diode is connected in series to wire A such it is reversed biased.

Sketch in in Fig. 3.2 the graph of the attractive force per unit length acting on wire A against time t from $t = 0$ ms to $t = 15$ ms. Numerical value of the force per unit length is not required.

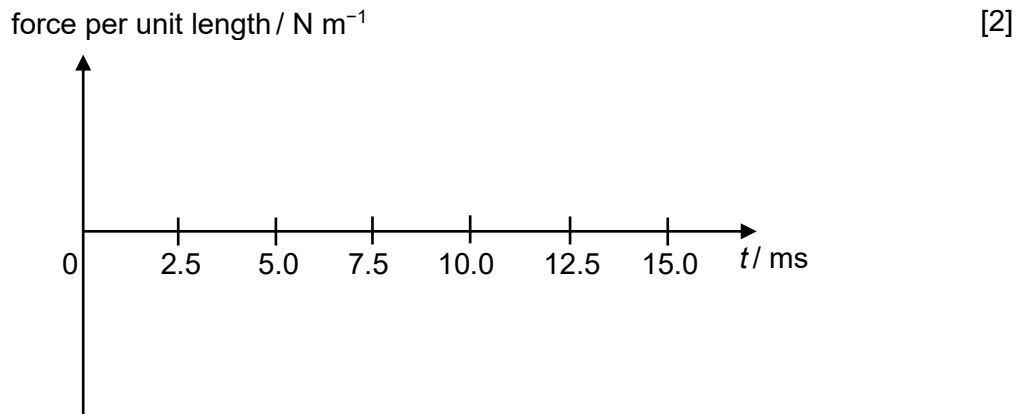


Fig. 3.2

3. The diode in (b)(ii)2. remains connected.

Determine the mean power dissipated across wire A given that the resistance of wire A is 15Ω .

mean power = W [1]