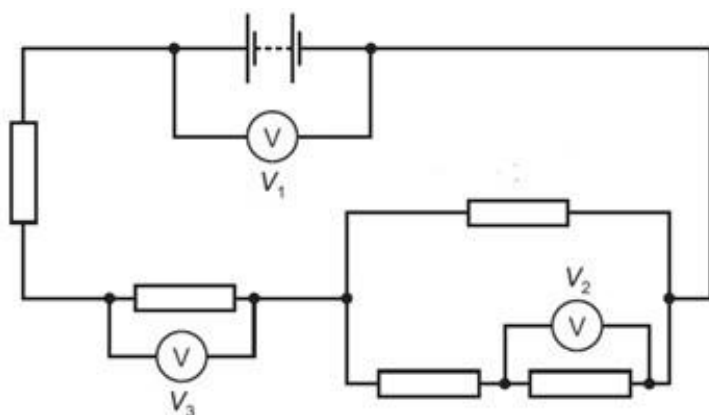


- 21 In the circuit shown, all the resistors are identical.



The reading V_1 is 8.0 V and the reading V_2 is 1.0 V.

What is the reading V_3 ?

- A** 1.5 V **B** 3.0 V **C** 4.5 V **D** 6.0 V