

- 21 A circuit is needed which switches on a warning lamp when the temperature of a thermistor is too high.

Which of the following circuits is suitable?

