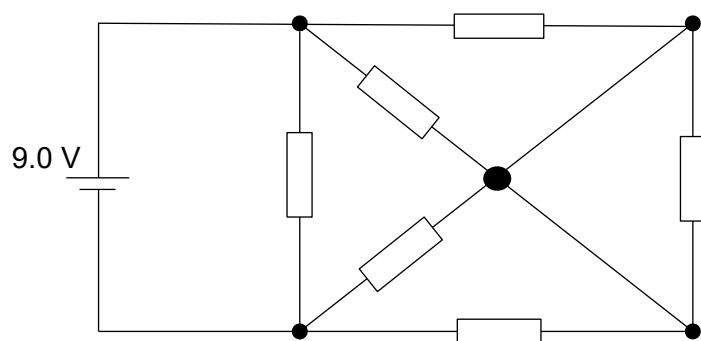


- 19** A cell of e.m.f. 9.0 V with negligible internal resistance is connected to 6 identical resistors, each of $10.0\ \Omega$ as shown below.



What is the current flowing through the cell in diagram above?

- A** 1.35 A **B** 1.80 A **C** 4.00 A **D** 5.45 A