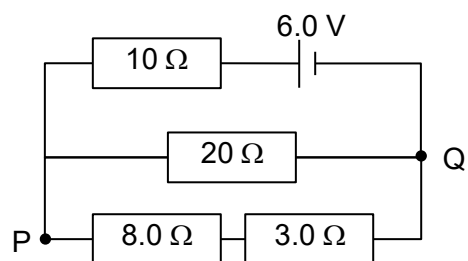


- 19 A battery with e.m.f. 6.0 V and negligible internal resistance is connected to several resistors as shown below.



What is the potential difference between P and Q?

- A** 1.6 V **B** 2.3 V **C** 2.5 V **D** 4.0 V

