

- 3 A 12 V cell of internal resistance  $30\ \Omega$ , a light-dependent resistor (LDR) and a  $600\ \Omega$  resistor are connected as shown in Fig. 3.1.

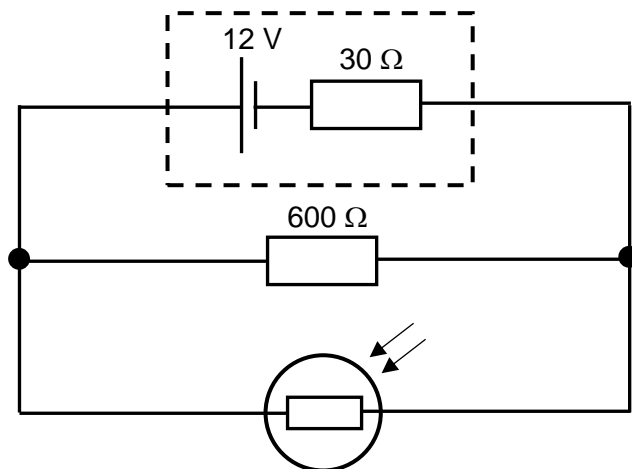


Fig. 3.1

- (a) In conditions of low intensity light, the resistance of the LDR is  $3000\ \Omega$ .

- (i) Show that the current through the LDR is  $3.8\ \text{mA}$ .

[3]

- (ii) Hence or otherwise, determine the power dissipated in the LDR.

power = ..... W [1]

- (b) The LDR is exposed to bright sunlight.

State and explain what would happen to the terminal potential difference.

.....  
 .....  
 .....  
 .....  
 ..... [3]