

- 4 A resistor of resistance of $8.2\text{ k}\Omega$ and a LDR (light dependent resistor) are connected in series, as shown in **Fig 4.1**. The resistance of the LDR when light is shone on it is $420\text{ }\Omega$ and when dark is $134\text{ k}\Omega$.

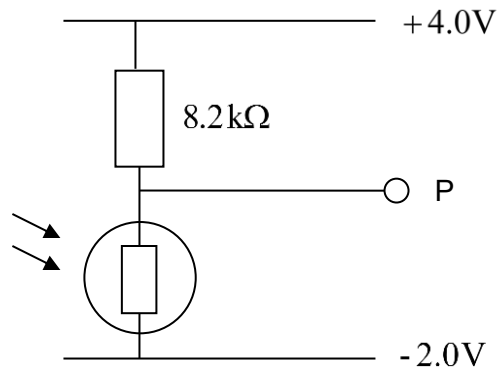


Fig. 4.1

- (a) Calculate the potential at point P when
- (i) light is shone on the LDR,

Potential = V [2]

- (ii) no light is shone on the LDR (dark).

Potential = V [1]

An alarm is now connected in parallel with the LDR in **Fig. 4.1** and a laser beam is directed at the LDR in a simple burglar alarm system. When a burglar blocks the laser that is shining continuously on the LDR, the alarm is triggered. Assume that the resistance of the alarm is very large.

- (iii) Explain clearly how the LDR is used to turn on/off the alarm in such a system.

.....

.....

.....

..... [2]

- (b) A circuit is set up as shown in **Fig. 4.2** below. The potentiometer wire has a resistance of $1.5\ \Omega$ and is $1.00\ \text{m}$ long. The movable contact J can be connected to any point along wire XY.

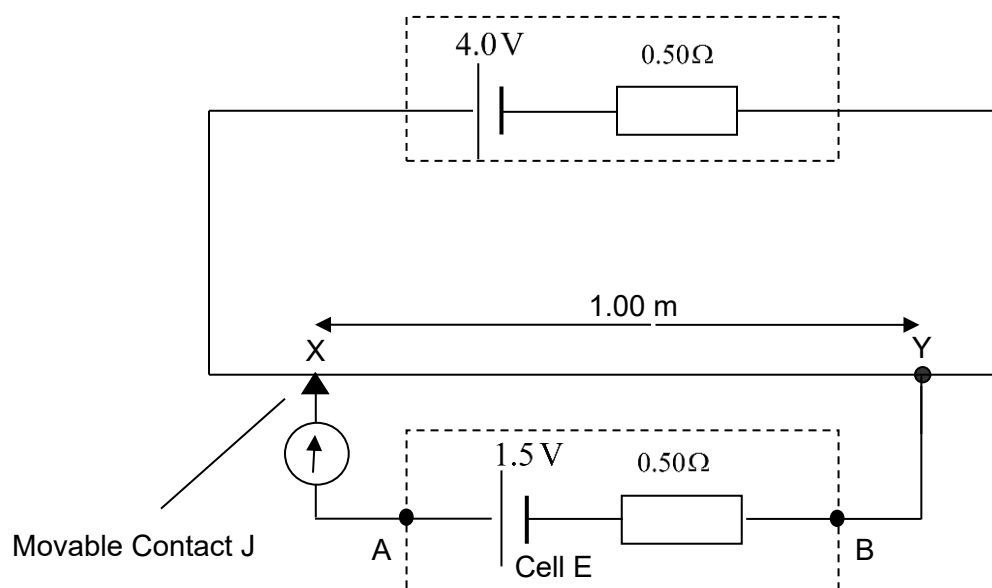


Fig. 4.2

- (i) Determine the distance of the contact J from X, such that there is no deflection in the galvanometer.

Distance = m [2]

- (ii) A $1.50\ \Omega$ resistor is connected across points A and B (in parallel with cell E). Determine the new distance of the contact J from X, such that there is no deflection in the galvanometer.

Distance = m [3]

