

- 4 A battery of electromotive force (e.m.f.) 3.0 V and negligible internal resistance is connected to a potentiometer, as shown in Fig. 4.1.

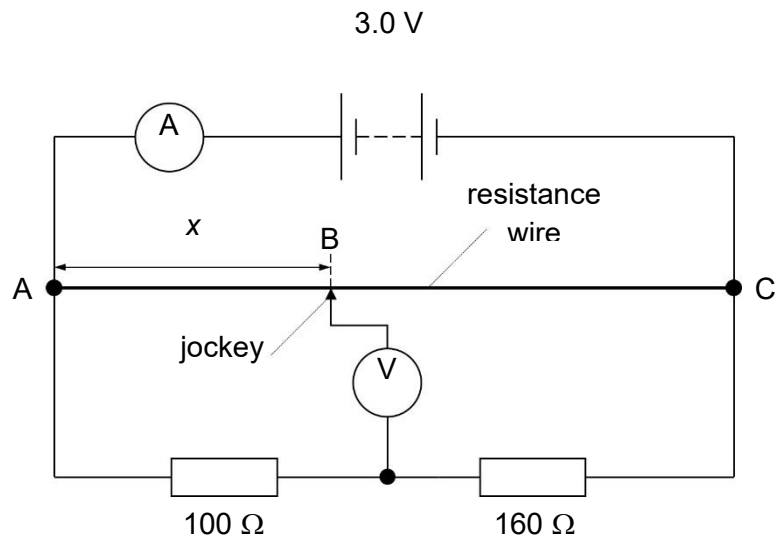


Fig. 4.1

The potentiometer consists of a 90 cm length of resistance wire AC. It is connected in parallel with a 100 Ω resistor and a 160 Ω resistor.

The jockey is in contact with the resistance wire at position B and the distance between A and B is x.

- (a) (i) The jockey is adjusted until the voltmeter reading is zero.

Determine the value of x.

$x = \dots\dots\dots$ cm [2]

- (ii) The ammeter reading is 234 mA.

Show that the resistance of wire AC is $13.5\ \Omega$.

[2]

- (iii) State and explain the change, if any, to the resistance determined in (a)(ii) if the battery has internal resistance.

.....

.....

.....

.....

..... [2]

- (b) An ideal diode is connected to the circuit and the battery is replaced by a 50 Hz sinusoidal alternating current (a.c.) power supply of peak voltage 12 V, as shown in Fig. 4.2.

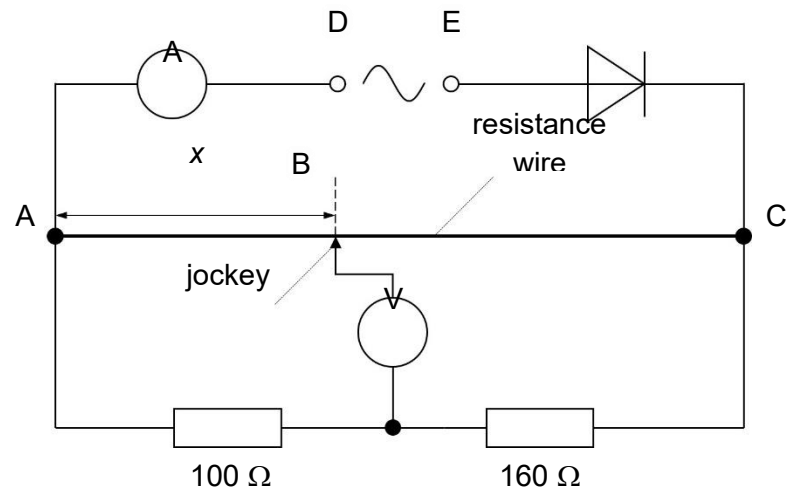


Fig. 4.2

- (i) Determine the mean power dissipated in the resistance wire AC.

mean power = W [2]

- (ii) Junctions D and E are connected to a cathode-ray oscilloscope (c.r.o.). The vertical scale of the c.r.o. is set to 4 V per division and the time-base is set to 5 ms per division.

Sketch the trace on the screen of the c.r.o. in Fig. 4.3.

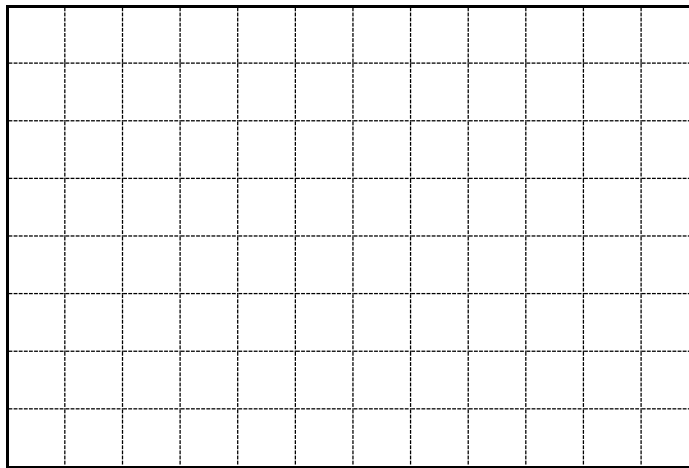


Fig. 4.3

[1]

