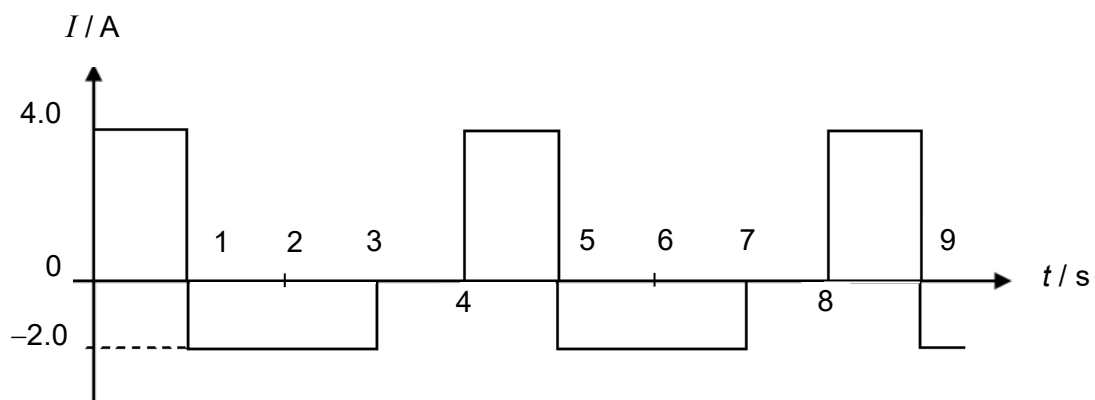


- 24** An alternating current with a rectangular waveform as shown in the diagram below flows through a  $11\ \Omega$  resistor.



What is the average power dissipated by the resistor?

- A** 0 W                      **B** 44 W                      **C** 66 W                      **D** 88 W