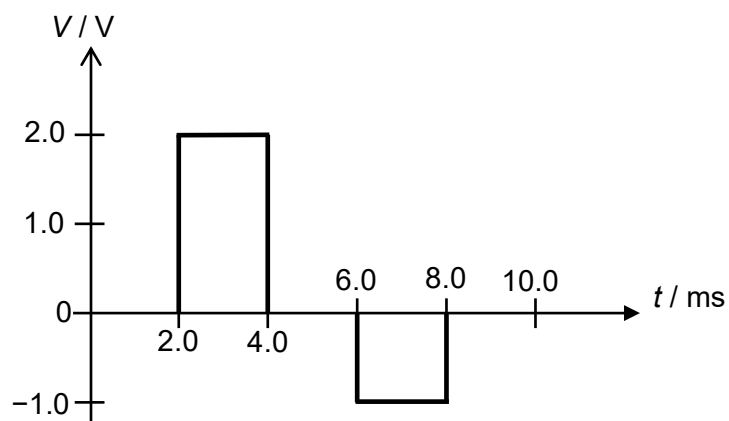


- 6 (a)** An alternating voltage of period 10 ms is being applied directly across a resistor of $5.0\ \Omega$ in a circuit. The variation with time t of voltage V is shown in Fig. 6.1.



0

Fig. 6.1

Calculate the steady voltage that would produce an identical heating effect in the same resistor.

voltage = V [2]

- (b) Explain why it is necessary to use high voltages for the efficient transmission of electrical energy.

.....
.....

.....
.....

.....
.....

.....
.....

.....
[2]

- (c) A sinusoidal voltage of 6.5 mV r.m.s. and 50 Hz is now connected to the primary coil of a transformer as shown in Fig. 6.2.

The transformer is assumed to be ideal and its turns ratio, $\frac{N_{\text{secondary}}}{N_{\text{primary}}}$ is 71.

The secondary coil is connected to a resistor R .

An average power of 0.040 W is produced in resistor R .

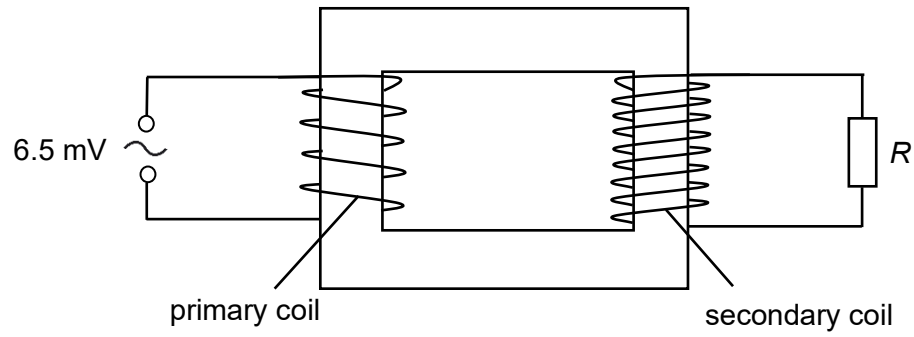


Fig. 6.2

- (i) Calculate the r.m.s output voltage supplied to resistor R .

r.m.s. voltage = V [1]

- (ii) In Fig. 6.3, sketch the variation with time t of the power P dissipated in the resistor R . Label all values on the axes.



Fig. 6.3

[2]

- (iii) An ideal diode is now connected to the secondary coil with resistor R as shown in Fig. 6.4.

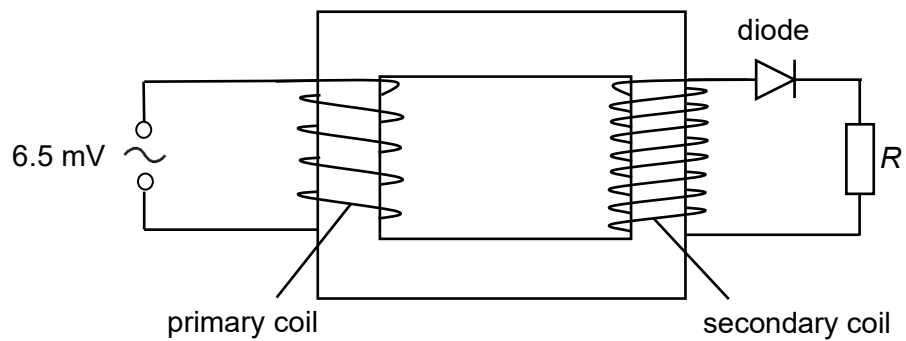


Fig. 6.4

Describe the variation with time of the

1. current flow through resistor R , and

.....
.....

.....
.....

.....
.....

.....
[2]

2. voltage across resistor R .

.....
.....

.....
.....

.....
[1]

[Total: 10]