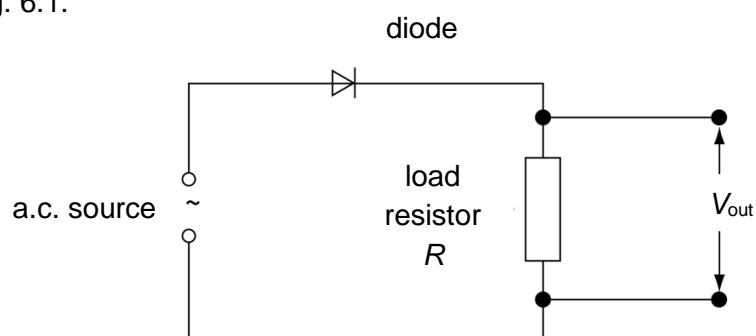


- 6 A load resistor  $R$  and a diode are connected to an alternating current (a.c.) source as shown in Fig. 6.1.



**Fig. 6.1**


The a.c. source supplies a voltage  $V$ , where

$$V = V_0 \sin 100\pi t$$

- (a) (i) Determine the period of variation of  $V$ .

period = ..... s [1]

- (ii) On Fig. 6.2, sketch the variation with time of  $V_{out}$ . Label the time axis.

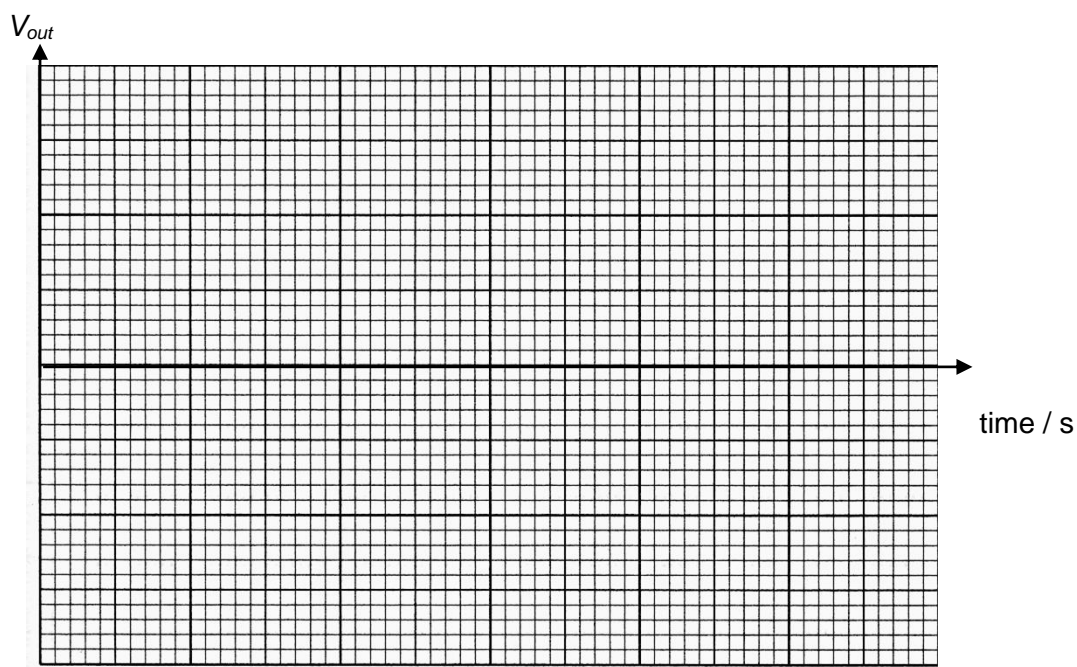

**Fig. 6.2**


[2]

- (b) (i) The mean power dissipated in load resistor  $R$  is found to be 40 W.

If  $R = 640 \, \Omega$ , determine the value of  $V_0$ .

$$V_0 = \dots\dots\dots \text{ V} \quad [3]$$

- (ii) On Fig. 6.3, sketch the variation with time of power dissipated across the load resistor  $R$ . Label both axes.

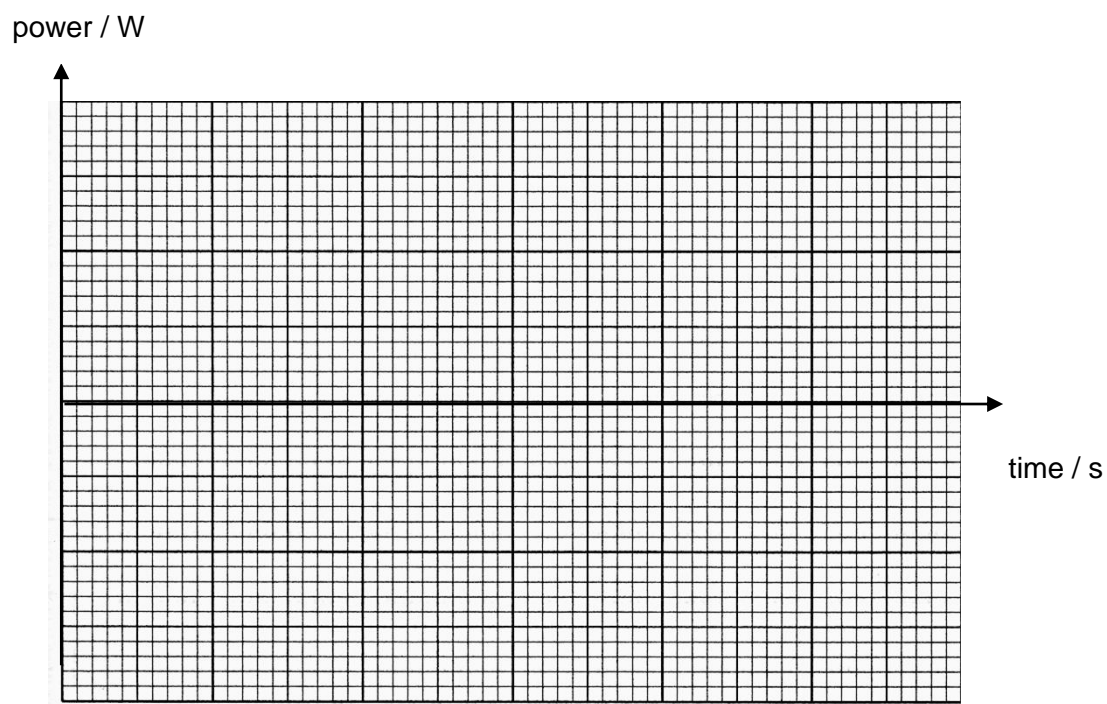

**Fig. 6.3**

[2]