

**20** In which circuit does the voltmeter not read 12 V?

