

- 21** Four different arrangements of identical resistors are connected to the same constant voltage power supply. An ammeter of negligible resistance is connected as shown in each arrangement.

In which arrangement will the ammeter show the minimum reading?

