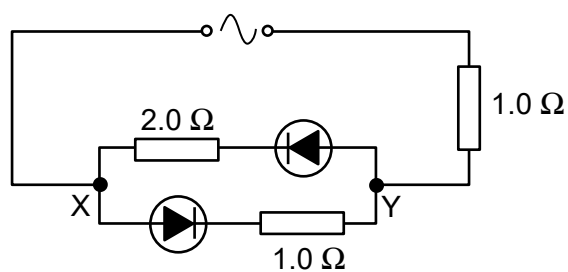


24 An a.c. source is connected to three resistors in the circuit below.



Which graph best represents the variation of the current I through the segment XY in the circuit with time t ?

