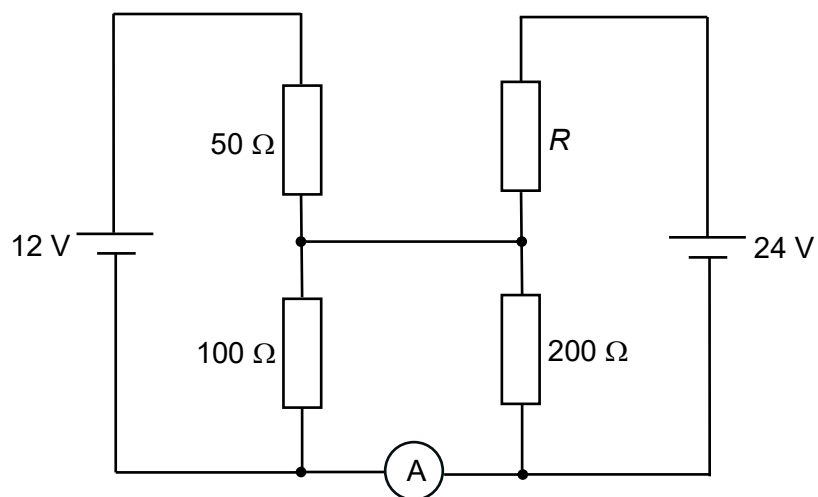


- 24 In the circuit shown, the ammeter reading is zero.



What is the value of resistance R ?

- A** 40 Ω **B** 100 Ω **C** 200 Ω **D** 400 Ω