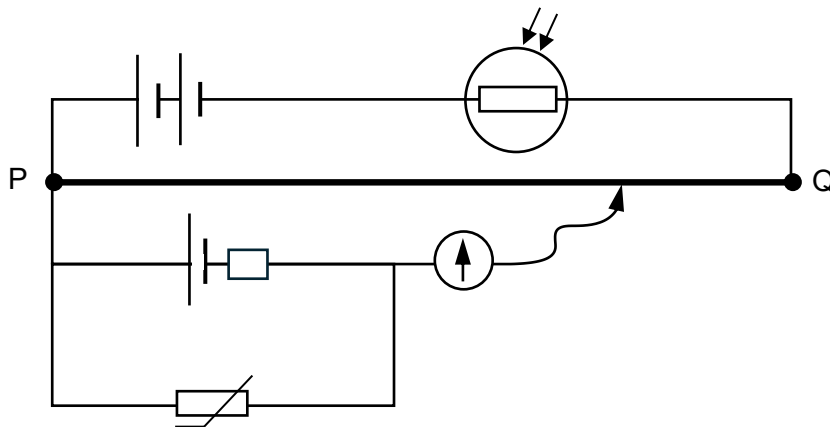


- 23** A NTC thermistor and a light-dependent resistor are connected in a potentiometer circuit. PQ is a resistance wire.



Which combination of temperature and lighting condition maximises the balance length?

	<u>temperature</u>	<u>lighting</u>
A	low	dark
B	low	bright
C	high	dark
D	high	bright

