

27 An alternating sinusoidal supply is connected to a resistor.

How does the power that dissipates in the resistor change when the frequency of the alternating supply doubles?

- A** Power drops to half the initial value.
- B** Power stays the same.
- C** Power doubles.
- D** Power quadruples.