

- 18** A circuit consists of a negative-temperature-coefficient (NTC) thermistor, a fixed resistor and a heater.

Which of the following arrangements allows the heater to be turned on when the temperature is low?

