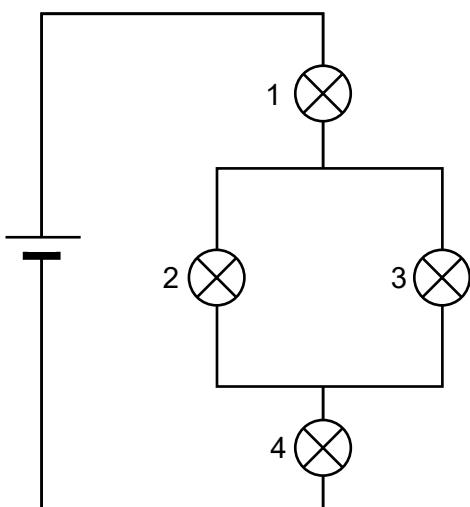


- 20** An ideal cell and four identical bulbs are connected as shown.



Bulb 3 is removed. Which of the following describes the changes in the brightness of bulbs 1, 2 and 4?

	Bulb 1	Bulb 2	Bulb 4
<b>A</b>	dimmer	brighter	dimmer
<b>B</b>	dimmer	brighter	brighter
<b>C</b>	brighter	dimmer	dimmer
<b>D</b>	brighter	dimmer	brighter