

- 6 (a) Using energy considerations, distinguish between *electromotive force* and *potential difference*.

.....

.....

.....

.....

.....

..... [2]

- (b) An electric hotplate is designed to operate on a power supply of 240 V and has two coils of wire of resistivity of  $9.8 \times 10^{-7} \Omega \text{ m}$ . Each coil of wire has a length of 16 m and cross-sectional area  $0.20 \text{ mm}^2$ .

- (i) For one of the coils, calculate


1. its resistance,

resistance = .....  $\Omega$  [2]

2. the power dissipation when a 240 V supply is connected across it.

power = ..... W [2]

- (ii) Fig. 6.1 shows how the two coils can be connected for the hotplate to operate at different powers.

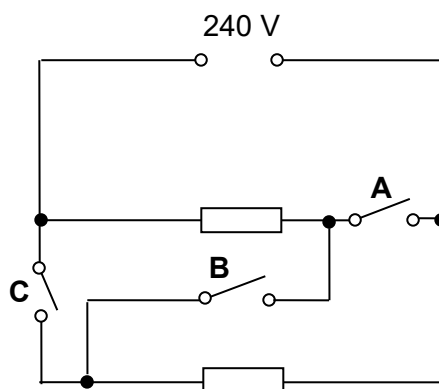

**Fig. 6.1**

On Fig. 6.2, fill up the table with “ON” or “OFF” to obtain the lowest and highest levels of operating power.

	switch A	switch B	switch C
Lowest			
Highest			

**Fig. 6.2**



