

- 25** An a.c. supply with peak voltage V_o and frequency of f delivers a mean power P when connected across a load resistor.

With the peak voltage now $\frac{1}{2} V_o$ and frequency $2f$, which expression gives the new mean power in the resistor?

A $P/4$

B P

C $\sqrt{2P}$

D $2P$