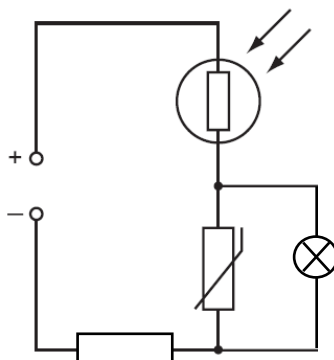


- 22** A filament lamp is connected into an electrical circuit with a negative temperature coefficient (NTC) thermistor and a light-dependent resistor (LDR).

Which pair of changes must cause the filament lamp to glow more brightly?



	light intensity incident on LDR	thermistor temperature
A	increase	decrease
B	increase	increase
C	decrease	decrease
D	decrease	increase