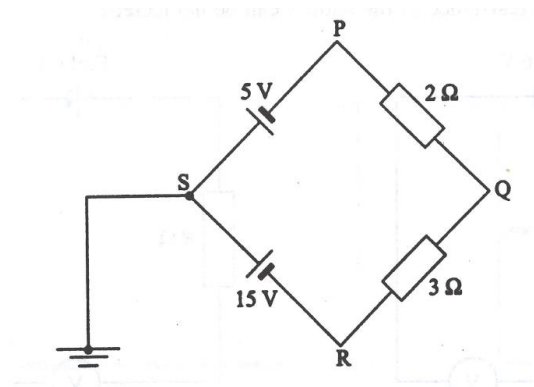


21 In the circuit below, the point S is earthed.



The electric potential at the points **P**, **Q** and **R** respectively are

	potential at <b>P</b>	potential at <b>Q</b>	potential at <b>R</b>
<b>A</b>	-5V	-15V	-10V
<b>B</b>	10V	1V	-15V
<b>C</b>	-5V	-9V	-15V
<b>D</b>	5V	-1V	10V