

- 20** A long wire of radius 1.5 mm and length 2.0 m carries a steady current 5.0 A. There are approximately  $1.5 \times 10^{24}$  mobile electrons in the wire.

What is the drift velocity of the electrons in the wire?

- A**  $4.2 \times 10^{-5} \text{ m s}^{-1}$     **B**  $7.2 \times 10^{-5} \text{ m s}^{-1}$     **C**  $7.2 \times 10^{-3} \text{ m s}^{-1}$     **D**  $2.9 \text{ m s}^{-1}$

- 21** A fixed resistor and a diode are combined by connecting them in series. The total potential