

- 6 A sinusoidal voltage supply of peak voltage 8 V and period of 1.2 s is connected to a circuit as shown in Fig. 6.1. The circuit consists of four resistors P, Q, R and S, which has a resistance of  $10\ \Omega$  each.

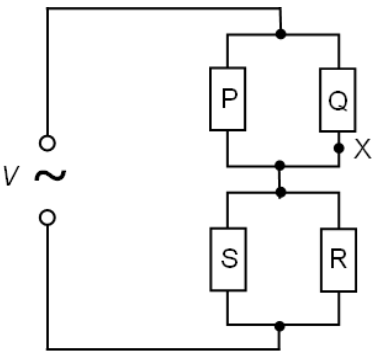


Fig. 6.1

- (a) Calculate the maximum potential difference across resistor P.

potential difference = ..... V [3]

- (b) Determine the peak power dissipated across resistor P.

peak power = ..... W [2]

- (c) An ideal diode is connected in series with resistor Q at point X.

On Fig. 6.2, sketch the variation with  $t$  of the p.d. across resistor Q for a time of 1.2 s. Add a scale to the y-axis.

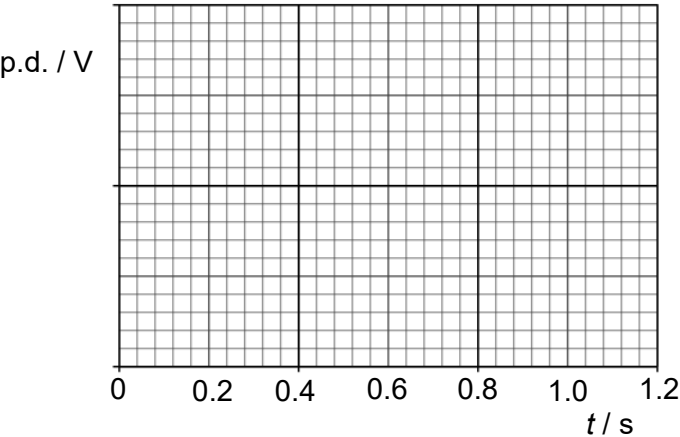


Fig. 6.2

[2]