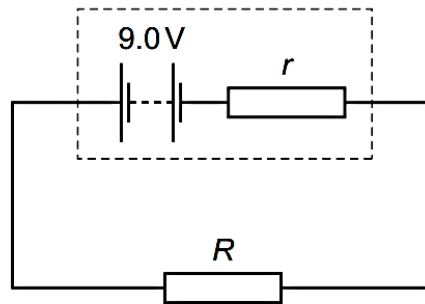


- 22** A simple circuit is formed by connecting a resistor of resistance  $R$  between the terminals of a battery of electromotive force (e.m.f.)  $9.0\text{ V}$  and constant internal resistance  $r$ .



A charge of  $6.0\text{ C}$  flows through the resistor in a time of  $2.0$  minutes causing it to dissipate  $48\text{ J}$  of thermal energy.

What is the internal resistance  $r$  of the battery?

- A**  $0.17\ \Omega$       **B**  $0.33\ \Omega$       **C**  $20\ \Omega$       **D**  $160\ \Omega$