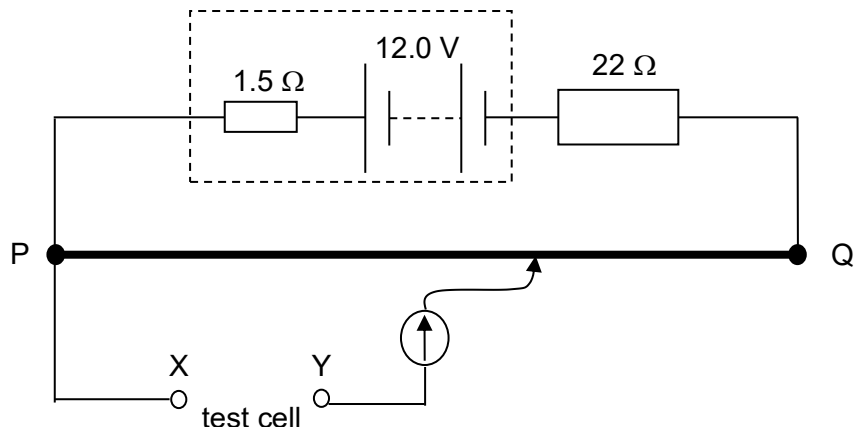


- 23** A student attempts to measure the e.m.f. of a test cell using a potentiometer circuit as shown below.



The wire PQ has a resistance of $3.0\ \Omega$ and the driver cell has an e.m.f. of $12.0\ \text{V}$ and internal resistance of $1.5\ \Omega$. He was unable to obtain an observable balance length on PQ when he connected the circuit. The tutor he consulted told him that the test cell has an e.m.f. of a few millivolts.

What could he do in order to obtain an observable balance length?

- A** Use a driver cell of e.m.f. $20\ \text{V}$.
- B** Reverse the polarity of the test cell at XY.
- C** Change the wire PQ to a wire of resistance $20\ \Omega$.
- D** Change the resistance of the connected resistor to $1\ \text{k}\Omega$.

